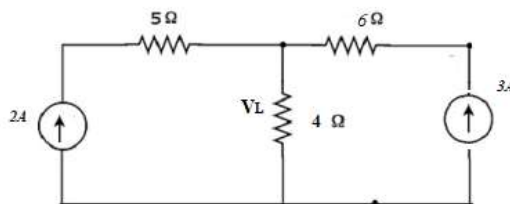


DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING  
19EE103T – BASIC ELECTRICAL ELECTRONICS AND COMMUNICATION  
ENGINEERING


**PART – A (1 MARKS)**

**UNIT – I DC CIRCUITS**

1. The path between any two nodes is called **Branch**  
(a) Branch (b) Node (c) Loop (d) Tree
2. In an electrical circuit, the algebraic sum of **Current** in a node is zero  
(a) Voltage (b) Current (c) Power (d) energy
3. In an electrical circuit, the algebraic sum of **Voltage** in a closed path is zero.  
(a) Voltage (b) Current (c) Power (d) energy
4. The **Energy** is given by the product of Power & Time.  
(a) Voltage (b) Current (c) Power (d) energy
5. Mesh analysis is used to solve **Current** variables of a circuit.  
(a) Voltage (b) Current (c) Power (d) energy
6. Mesh equation are **KVL** equation of a circuit.  
(a) KVL (b) KCL (c) Ohms Law
7. The solution of a mesh basis matrix equation  $IR=V$  will be in the form  **$I=V/R$**   
(a)  $I=V/R$  (b) R (c) V (d) I
8. Node analysis is used to solve **Voltage** variables of a circuit.  
(a) Voltage (b) Current (c) Power (d) energy
9. Node equation are **KCL** equation of a circuit.  
(a) KVL (b) KCL (c) Ohms Law
10. The voltage  $V_L$  in the circuit shown




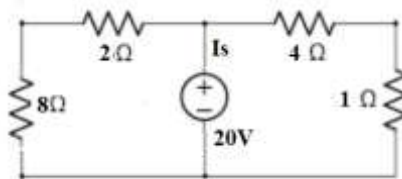- (a) 4v (b) 8v (c) 12 v (d) **20 v**
11. The current  $I_s$  delivered by the voltage source in the circuit shown




- (a) **6 A** (b) 5A (c) 4A (d) 2A

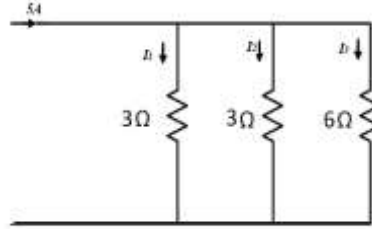12. In fig, the current  $I_1, I_2$  &  $I_3$  respectively are



- (a) 1.5 A , 1.5 A, 2 A (b) 1A, 1A, 3A (c) 1A, 2A, 3A (d) **2A, 2A, 1A**

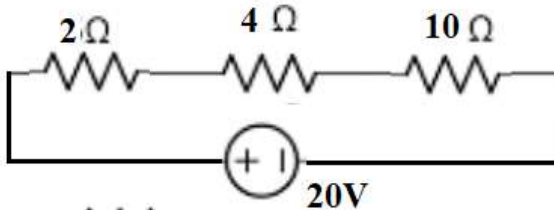13. In fig, the current  $V_1, V_2$  &  $V_3$  respectively are




- (a) 4V, 6V, 10V (b) 3.5V, 6.5V, 10V (c) **2.5V, 5V, 12.5V** (d) 2V, 6V, 12V

14. A voltage source connected in series with a resistor can be converted to a?

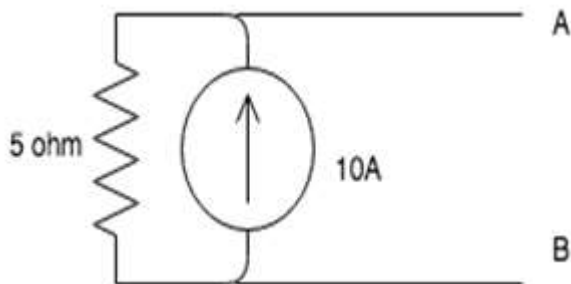- a) Current source in series with a resistor  
 b) **Current source in parallel with a resistor**  
 c) Voltage source in parallel with a resistor  
 d) Cannot be modified

15 Find the value of voltage once source transformation is applied to the circuit.



- a) 10V b) 30V c) **50V** d) 70V

## UNIT 2(AC Circuits & Transformer)

1. In a series RLC circuit the phase difference between current in the circuit and the voltage across the capacitor is  
(a)  $0^\circ$  (b)  $90^\circ$  (c)  $180^\circ$  (d)  $360^\circ$
2. In a series RLC circuit the phase difference between current in the circuit and the voltage across the inductor is  
(a)  $0^\circ$  (b)  **$90^\circ$**  (c)  $180^\circ$  (d)  $360^\circ$
3. In a series RLC circuit the phase difference between current in the circuit and the voltage across the resistor is  
(a)  $0^\circ$  (b)  $90^\circ$  (c)  $180^\circ$  (d)  $360^\circ$
4. Find the total voltage applied in a series RLC circuit when  $i=3\text{mA}$ ,  $V_L=30\text{V}$ ,  $V_C=18\text{V}$  and  $R=1000\text{ ohms}$ .  
a)  $3.95\text{V}$  b)  **$51\text{V}$**  c)  $32.67\text{V}$  d)  $6.67\text{V}$
5. In an RLC circuit, the power factor is always \_\_\_\_\_  
a) Positive b) Negative c) **Depends on the circuit** d) Zero
6. In an RLC series phasor, we start drawing the phasor from which quantity?  
(a) Voltage (b) Resistance (c) Impedance (d) **Current**
7. In an RLC circuit, which of the following is always used as a vector reference?  
a) **Voltage** b) Resistance c) Impedance d) Current
8. What is the correct expression for the phase angle in an RLC series circuit?  
a)  **$\phi = \tan^{-1}(X_L - X_C)/R$**  (b)  $\phi = \tan^{-1}(X_L + X_C)/R$   
c)  $\phi = \tan(X_L - X_C)/R$  d)  $\phi = \tan^{-1}(X_L - X_C)$
9. Which of the following is not an ac waveform?  
a) sinusoidal b) square c) **constant** d) triangular
10. If supply frequency of a transformer increases, the secondary output voltage of the transformer  
(a) Increase (b) Decrease (c) **Remain the same** (d) Any of the above
11. The open circuit test in a transformer is used to measure  
(a) Copper loss (b) Winding loss (c) Total loss (d) **Core loss**
12. Lamination of transformer core is made of  
(a) Cast Iron (b) **Silicon Steel** (c) Aluminum (d) Cast Steel
13. Breather is provided in a transformer to  
(a) **Absorb moisture of air during breathing** (b) provide cold air in the transformer  
(c) The filter of transformer oil (d) None of the above
14. Which of the following losses varies with the load in the transformer?  
(a) Core loss (b) **Copper loss** (c) Both core & copper loss (d) None of the above
15. A transformer transforms  
(a) Current (b) Voltage & current (c) Frequency (d) **Voltage**